



System Solution Guide

Industrial Motor Drive



onsemi.com



Table of Contents

[Get Latest Version](#)

Overview

Application

03

System Description

Opportunities for CO2 Reduction

04

Commonly Used Motor Types

05

Solution Overview

Motor Drive Top Level Topology

08

Motor Drive Architecture

09

Power Factor Correction

10

Inverter Switch Variety

11

IGBT – Cost-effective High-voltage Switch

12

EliteSiC MOSFET – Best Performance

13

Intelligent Power Modules – Highly Integrated and Reliable

14

Power Integrated Modules (PIM) – Highest Power

15

Elite Power Simulator Powered by PLECS®

16

Gate Drivers – Importance of Correct Gate Drive Voltage

17

Recommended Products

18

Complementary Products

21

Development Tools and Resources

23

Technical Documents

24

Overview

Industry

Industrial – Industrial Drives, Robotics

Applications

Electric motors will continue to be widely used. They can be used in small home appliances, in industrial manufacturing and in heavy-duty applications. Their versatility allows them to be used for almost any purpose. Electric motors account for approximately half of the world's electricity consumption, with an ever-rising trend. Nowadays, with the intensifying drive to reduce carbon emissions, it is becoming increasingly crucial to enhance efficiency, through the implementation of novel control algorithms, utilization of new, more efficient motor architectures and by the incorporation of modern semiconductor technologies.

Industrial motor drives are the backbone of contemporary global industry. They account for almost two-thirds of the energy consumed in all industrial applications.

With the regulations becoming increasingly stringent, the necessity for substantial energy savings in industrial drives is becoming increasingly apparent. AC motors can typically be driven directly from the mains AC supply. However, for enhanced efficiency and superior control, a variable frequency drive implementation is required.

An industrial drive system that uses variable frequency drive (VFD) is more efficient than system utilizing conventional throttle control. onsemi offers a wide variety of products for VFD including MOSFETs, IGBTs, diodes, power integrated modules (PIM) and intelligent power modules (IPM).

Other components and technologies used in the subsystems include gate drivers, operational amplifiers, position sensors, temperature sensors and other used for control and sensing

The efficiency and longevity of motor drives are increased by usage of modern semiconductors and novel motor architectures.

Industrial drives are employed in a multitude of industrial sectors including process automation, fan control, liquid and gas pumps, robotics, material handling, machine tools, the oil and gas industry, and others.



System Description

Opportunities for CO2 Reduction

The utilization of electric motors ranges from small to heavy-duty applications. Various sources indicate that electric motor drives consume approximately half of the globally generated electricity. Industrial applications account for almost one-third of the world's electricity production. It is expected that the increasing automation in the industrial field will lead to an increase in the number of industrial motor systems. Nowadays, sustainability and energy efficiency are becoming important topics of discussion. It is therefore crucial to both update existing solutions and newly deployed systems achieve the highest possible efficiency.

The market of industrial motor drives is expected to grow at an average compound growth rate (CAGR) of 5 to 5.5% from 2024-2029, from 25.5 billion to 32.7 billion \$. Incentives to grow include rapid industrialization in developing economies. The market is currently pushed into process optimization and energy efficiency. Electric drives tend to be much more efficient and require less maintenance than other solutions, such as gas turbines.

The 2020 Motor System Market Assessment (MSMA) report indicates that motor drive systems in the USA offer more than 5 billion USD and more than 43 million metric tons of CO2 annual savings opportunity. The main points for improvement are controllers and motors.

The motor controllers can be improved by implementing a variable frequency drive (further explained below), which significantly improves efficiency under varying loads. In the past a lot of deployed systems were overrated. This resulted in a longer operational lifetime, but on the other hand it decreased the overall efficiency of the system. Implementing load matching and variable frequency drive could achieve an efficiency increase of more than 10%.

The aforementioned 2020 MSMA report indicates that the incorporation of more efficient motors, such as permanent magnet synchronous motors, can result in the annual saving of 45,000 GWh of electricity in the United States alone. The integration of wide bandgap (WBG) semiconductors further increases the efficiency of the system, although at the cost of higher initial investments. Their other advantages include higher operating temperature, higher operating voltages and higher switching frequencies, which can reduce the size and cost of passive components.

Variable Frequency Drive

The majority of modern three-phase motors, which are widely used in robotics, industrial and other demanding applications, are driven by power switches. The systems commonly use a pulse width modulation (PWM) signal to determine the commutation between the ON and OFF states. This is called variable frequency drive (VFD), and it is much more efficient than conventional throttle control, saving energy mainly with varying load.

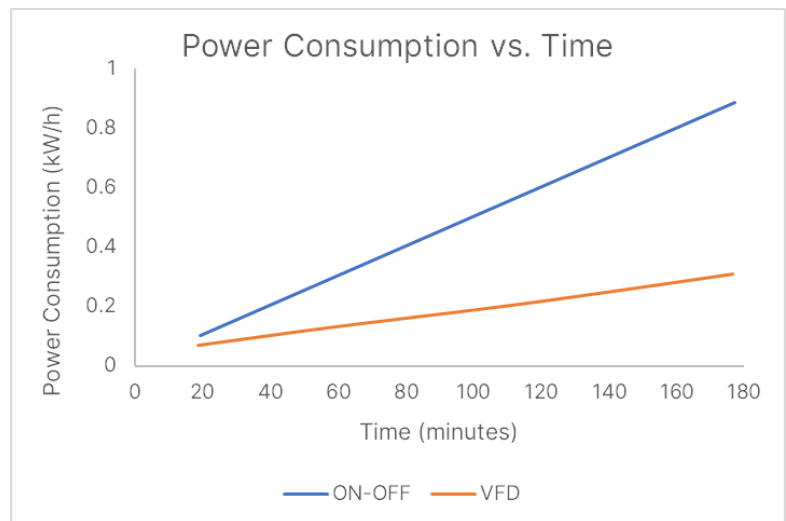


Fig.1: Effect of variable frequency drive on power consumption

System Description

Commonly Used Motor Types

Previously widely used DC motors use mechanical brushes for commutation between stator and rotor, which causes higher noise, a greater need for maintenance, lower efficiency and inferior thermal performance. In contrast, brushless motors are electronically commutated and are therefore more efficient, quieter, require little to no maintenance and have a longer lifetime. However, their control is more complicated. The three most prevalent types of the AC motors are: AC induction motors (ACIM), permanent magnet synchronous motors (PMSM), and brushless DC (BLDC) motors.

AC induction motors consist of stator with multiple windings and a rotor constructed from multiple conductive bars. When an AC current is applied to the stator windings, a rotating electromagnetic field is created in accordance with Faraday's Law. This rotating electromagnetic field induces currents in the rotor windings. The induced currents in the rotor create magnetic field that reacts against the stator field. The direction of the induced magnetic field reacts against the stator field producing a force that causes the rotor to rotate in the direction of the stator's magnetic field. Since rotation at synchronous speed does not induce rotor current, an induction motor always operates slightly slower than synchronous speed. This difference between synchronous speed and operational speed of the rotor is referred to as "slip" or slip angle. The typical slip value is between two and six percent. This is the reason why ACIMs are considered asynchronous. The speed of the AC induction motors can be controlled by modifying the frequency of the input current, for instance by utilizing variable a frequency drive (VFD).

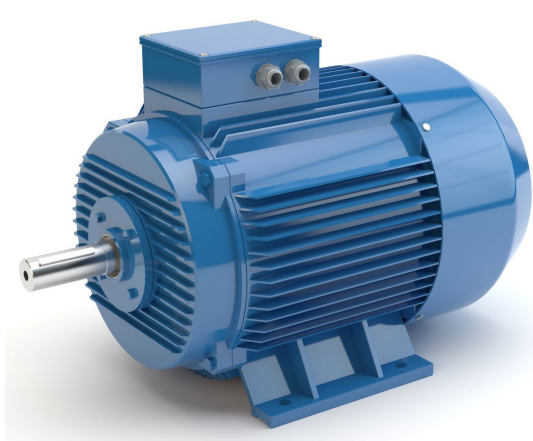


Fig.2: AC induction motor

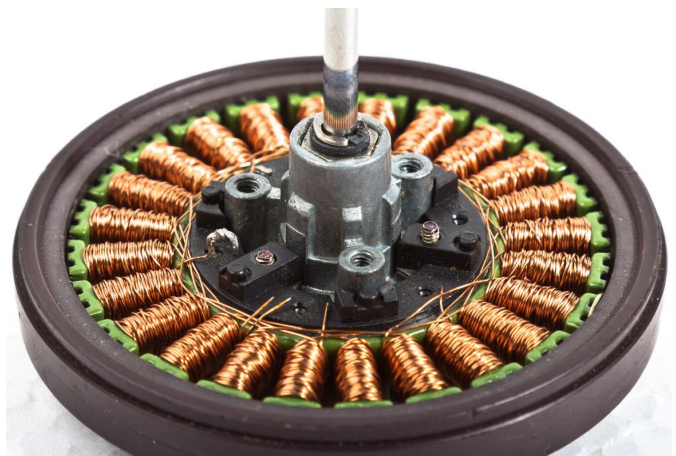


Fig.3: Brushless DC motor

Permanent magnet synchronous motors (PMSM) and brushless DC (BLDC) motors utilize the same stator as ACIM, but their rotors contain permanent magnets. This eliminates the need for induction, thereby increasing efficiency. In this type of motor, the rotor speed is equal to the speed of the stator's electromagnetic field, hence the synchronous operation. The distinction between PMSM and BLDC lies in their respective control and their back-electromotive force (BEMF) response. The BLDC BEMF response is trapezoidal while that of PMSM is sinusoidal.

ACIM and PMSM/BLDC are commonly used in heavy-duty applications like conveyor belts, material handling systems, pumps and compressors. They are ideal for continuous operation and when precise speed and torque control are required. One disadvantage of these motors is their higher cost due to the inclusion of permanent magnets.

System Description

Table 1: Comparison of AC induction motors and permanent magnet synchronous/brushless DC motors

Type	Pros	Cons
AC Induction Motor	<ul style="list-style-type: none">• Low cost• Self-starting• Reliable• Easy to control• Easy brake implementation• More peak power	<ul style="list-style-type: none">• Higher losses• Heavier• Loss of torque at high speeds
Permanent Magnet Synchronous/ Brushless DC Motors	<ul style="list-style-type: none">• Compact size• Able to stop frequently without overheating• Lightweight• Magnetic field intrinsic to permanent magnets	<ul style="list-style-type: none">• Expensive• Lower efficiency at high speeds due to eddy currents• No easy way to change magnetic field strength• More complicated control

Stepper motors and servo systems are used for the precise positioning and controlled movement. They are widely used in applications requiring the holding and positioning. They are employed to power robot arms, assembly lines, lift-assist devices and other similar applications. The systems are characterized by their high degree of accuracy and substantial repeatability.

A stepper motor is typically composed of a rotor with a permanent magnet and multiple teeth, which determine the number of steps. The stator also contains teeth, although fewer than those on the rotor. These are distributed in a way that some are aligned with those on the rotor, and some are misaligned. The stator coils are divided into two independent sets. When energized, the coils create a magnetic field which causes the rotor to make exactly one step by aligning the teeth. By repeatedly energizing the two sets of coils, a highly precise motion can be achieved without the need for any feedback, which is referred to as open loop control.



Fig.4: Stepper motor – notice the teeth on stator and on rotor

Stepper motor drives can be unipolar or bipolar. Bipolar stepper motors permit the current to flow in both directions and require a full-bridge inverter to drive each of the two sets of windings. In contrast, unipolar stepper motors require only one direction of current flow, simplifying their control. Such motors may be controlled by simple high- or low-side switches, offering a more cost-effective option.

A servo motor operates within a closed-loop control system. The system employs feedback from an encoder to compare the actual position of the motor to the required value. The closed-loop ensures precise positional control. A Servo motor system consists of three main parts: the motor, the feedback device and the control circuit. The motor generates the mechanical power and can be either brushed DC, or BLDC, PMSM or even ACIM. The feedback device provides information about the motor's position, torque and speed. The control circuit compares the required position with the actual position and adjusts the output to correct any discrepancy.

System Description

Table 2: Comparison of stepper motors and servo motor systems

Type	Pros	Cons
Stepper Motor	<ul style="list-style-type: none">• Simple to control• High torque at low speed and when stationary• Less expensive	<ul style="list-style-type: none">• Less torque at high speed• May lose steps at high speeds• Can be noisy
Servo Motor	<ul style="list-style-type: none">• Continuous rotation• Higher precision due to closed-loop• High torque at wide range of speeds	<ul style="list-style-type: none">• More expensive• More complex• Limited torque when stationary

Motor Control Techniques

The trapezoidal control algorithm also known as the six-step control, is the simplest control algorithm. It involves the current flowing through two phases at a time, with the third phase floating. There are six discrete states applied to the motor. This method generates high torque, but it has higher noise and vibrations than other more advanced algorithms.

In sinusoidal control the current waveform applied to the motor windings is sinusoidal. This results in reduced torque ripple. However, it is more complex to implement since it requires precise synchronization and identifying the rotor position.

Field oriented control (FOC) provides better efficiency at high speeds compared to sinusoidal control. It offers superior performance on dynamic loads in comparison to the aforementioned techniques. It optimizes motor torque by maintaining ninety-degree alignment between the stator and rotor throughout the entire commutation, reducing torque ripple and resulting in smoother, quieter rotation.

Rotor Position Detection

The most common method of detecting rotor position is through the utilization of Hall effect sensors. As the rotor passes the Hall effect sensor, it provides information about the position of the magnet poles to the controller. The Hall effect sensors are typically distributed at 120 degrees apart.

In sensorless applications, the back-electromotive force (BEMF) is measured to determine the rotor position and switching signals. A comparison of Hall sensors and back emf can be seen in Figure 5.

Other possibilities include the use of optical or inductive sensors to obtain accurate information about the position of the rotor.


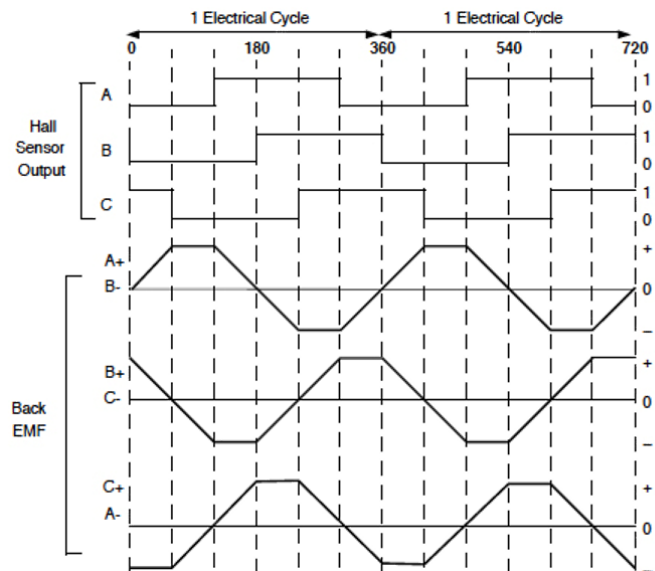


Fig.5: Comparison of Hall sensor output and measured back electromotive force

Solution Overview

Motor Drive Top Level Topology

Block diagram below represents industrial motor drive solution recommended by **onsemi**. Most important building block is AC-AC stage. In the past considerable number of motors were directly powered from mains, but it is more efficient to use AC/DC converter and then inverter stage. Other important parts include control unit, which contains algorithm and controls whole system, sensing which delivers feedback and auxiliary power supply providing low voltage rails.

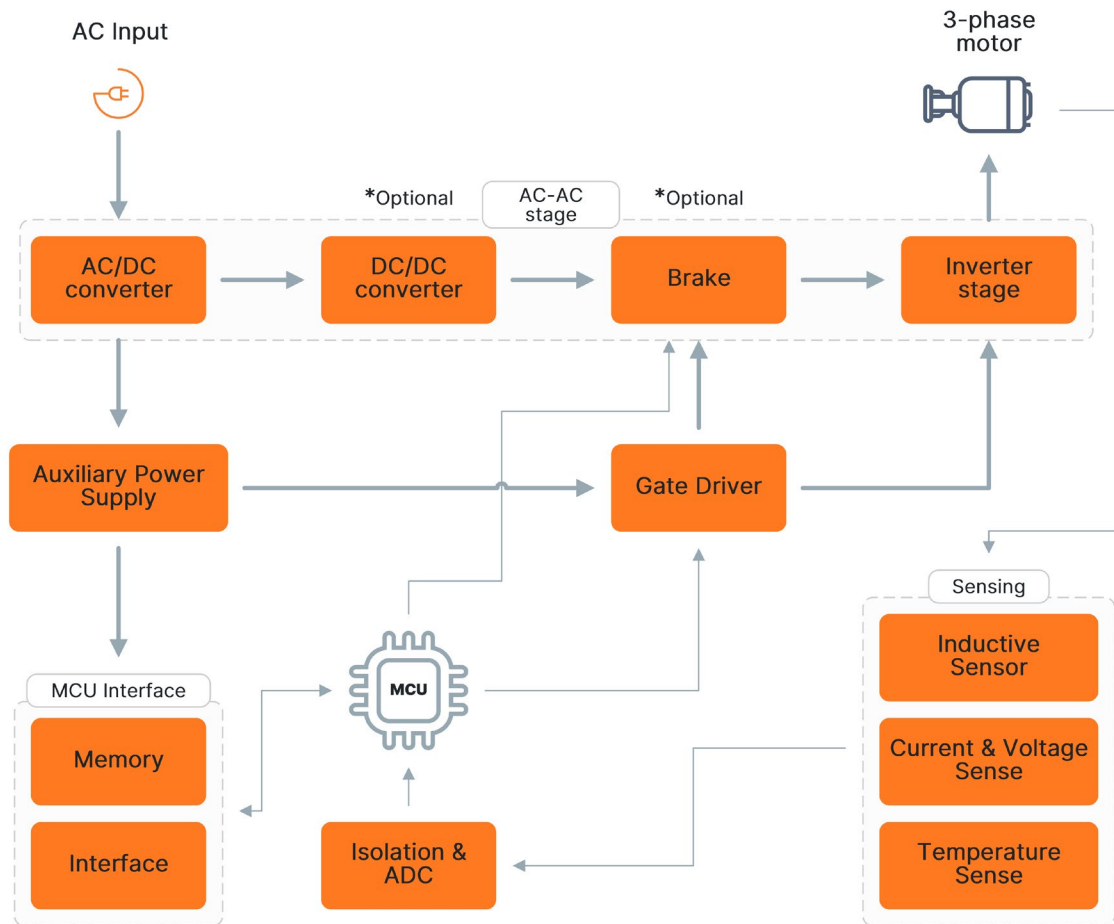

Use our Interactive Block Diagrams Tool



Open IBD Tool

Solution Overview

Motor Drive Architecture

The general architecture of a grid-powered motor control circuit consists of the following elements: a rectifier, power supplies, sensing, control hardware and a power stage.

The rectifier stage is responsible for converting alternating current (AC) into direct current (DC). This can be achieved using a simple diode bridge, but in order to increase the efficiency and power factor (thus reducing reactive power) of the system, power factor correction stage can be used. An optional DC-DC stage is used to convert the DC voltage to the voltage required by the motor. Auxiliary power supplies convert the AC input or DC bus to different low voltages into supply control hardware (MCU, memory, interfaces, etc.) and also gate drivers.

A brake circuit is utilized to dissipate energy during deceleration. When the motor is disconnected from the power supply, it starts to act as a generator. Dynamic braking takes advantage of a braking resistor connected in series with a power switch (typically an IGBT), to dissipate the power from the motor.

An inverter is composed of power switches that transfer power to the motor. Depending on the power level, they can be Si MOSFET, IGBT or silicon carbide (SiC) MOSFET. They can be discrete, in the form of a power module or modules with integrated gate drivers.

In order to perform accurate electronic commutation, it is necessary to ascertain the position of the rotor. This has been traditionally achieved by utilizing a Hall sensor. More novel solutions use optical or inductive sensors, while some solutions skip the sensor and measure back electromotive force. Inductive position sensors such as the NCS32100 are especially useful during start-up, when the exact position of the rotor needs to be known. It is possible that the position was altered during the period of downtime, and the system is therefore unable to rely on the last known state.

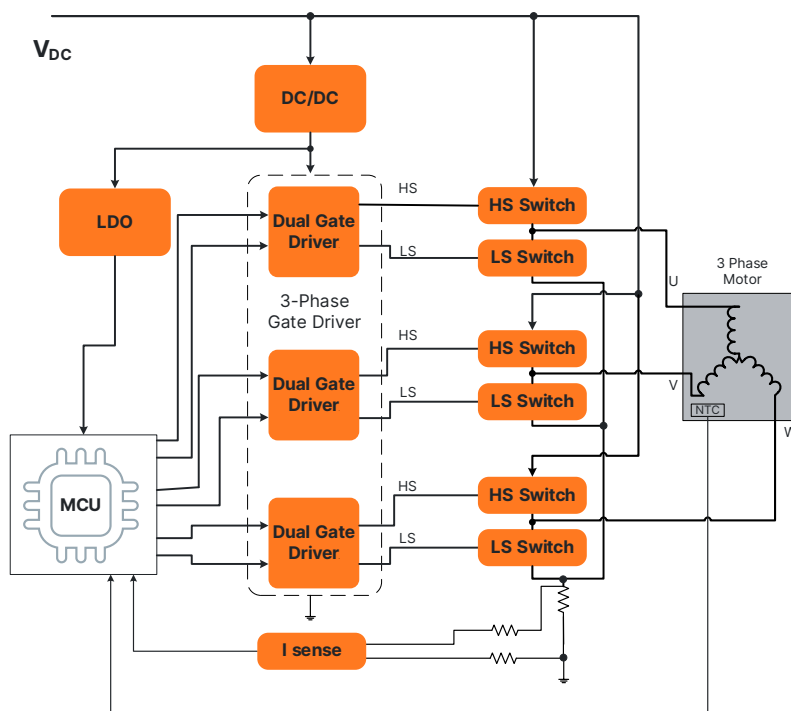


Fig.6: Example of three phase motor discrete control and power stage block schematic

Inductive Sensing NCS32100

- Calculates position and velocity
- **Absolute encoder** – no movement needed to determine its position
- 6,000 RPM full accuracy (45,000 maximum RPM)
- +/- 50 arcsec (0.0138 degree) or better accuracy for a 38mm sensor – see figure 16
- Can differentiate and reject the vibrations from the rotational movement
- Integrates CortexM0+ MCU – highly configurable
- Cheaper alternative for a wide range of the optical encoders

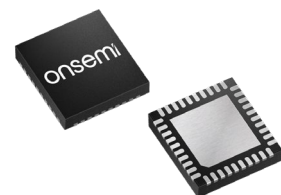


Fig.7: QFN-40 package

Solution Overview

Power Factor Correction

The power factor correction (PFC) stage is an AC/DC converter. Its objective is to shape the input current to match the shape of the input voltage. This reduces the harmonics and improves the efficiency.

The PFC stage is typically implemented by inserting a boost converter stage between the rectifier bridge and the input capacitor. In single-phase applications, interleaved boost (Figure 7) or totem pole PFC can be used. These topologies can usually be used for powers up to 2 kW depending on the used controller and conduction mode.

Totem pole PFC (figure 10) replaces bridge diodes with active switches to reduce losses. The totem pole PFC stage consists of a fast-leg (switched at high frequency, 100 kHz or more) and a slow-leg (switched at mains frequency). In the fast-leg, wide bandgap semiconductors are preferred, as they allow higher switching frequency, thus reducing the size of the passive components. As a slow-leg switch, an IGBT can be used.

For three-phase high-power applications, the Vienna rectifier, active front end, or power module with integrated PFC is ideal. The Vienna rectifier (Figure 8) has high efficiency but higher cost due to the number of required power switches and more complicated control. For further insight into various PFC topologies refer to [Demystifying Three-Phase Active Front End or Power Factor Correction \(PFC\) Topologies](#).

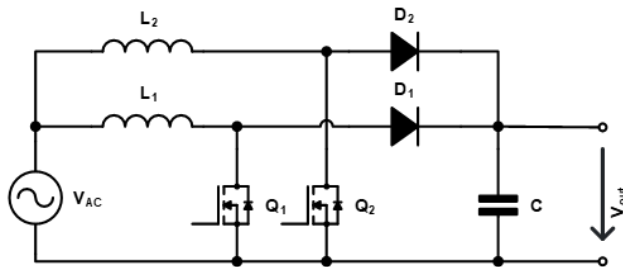


Fig.7: Single-phase two-channel interleaved boost converter

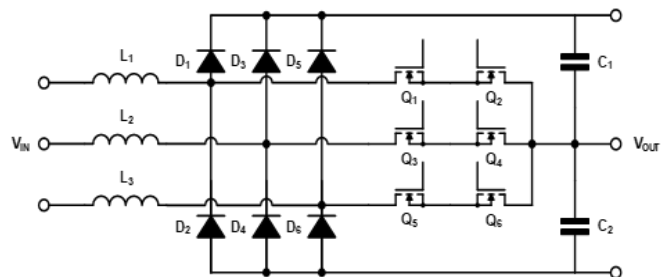


Fig.8: Three phase Vienna rectifier

Power Factor Controllers [NCP1681](#)

Bridgeless Totem Multi-Mode PFC Controller

- Fixed frequency CCM (Constant Conduction Mode) with Constant on-time CrM and valley switching frequency foldback
- Proprietary Current Sense Scheme
- Proprietary valley sense scheme
- Ideal for high power: Multi-Mode applications up to 1kW, CCM >2.5kW
- SOIC-20 package

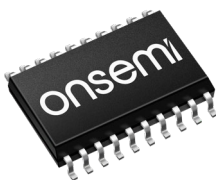


Fig.9: SOIC-20 package

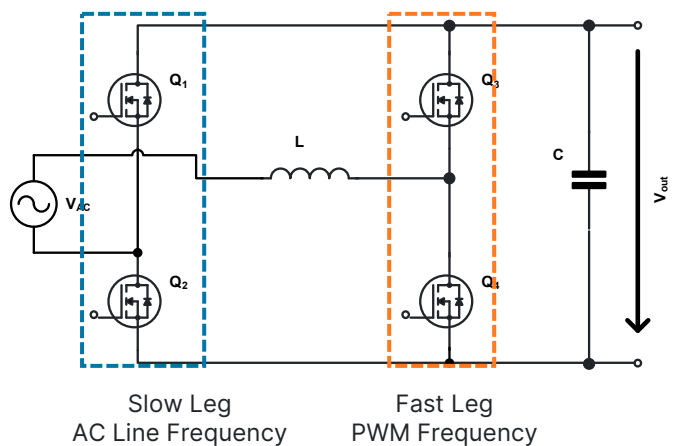


Fig.10: Totem Pole PFC schematic

Solution Overview

Inverter Switch Variety

A motor control system can be designed using discrete components (IGBT, Si MOSFET, SiC MOSFET, diodes, gate drivers, etc.) or power modules, which integrate multiple parts. These modules can integrate a three-phase half bridge, one half bridge, or even include a brake, PFC, or gate driver in one package.

Suitable power switch from onsemi can be selected from figure 11, depending on the application, desired power, and motor voltage. Discrete solutions using IGBT or SiC can be utilized for single phase applications up to approximately 5 kW. Power modules can be divided into power integrated modules (PIM), and the intelligent power modules (IPM). The use of modules offers numerous advantages over the discrete solutions.

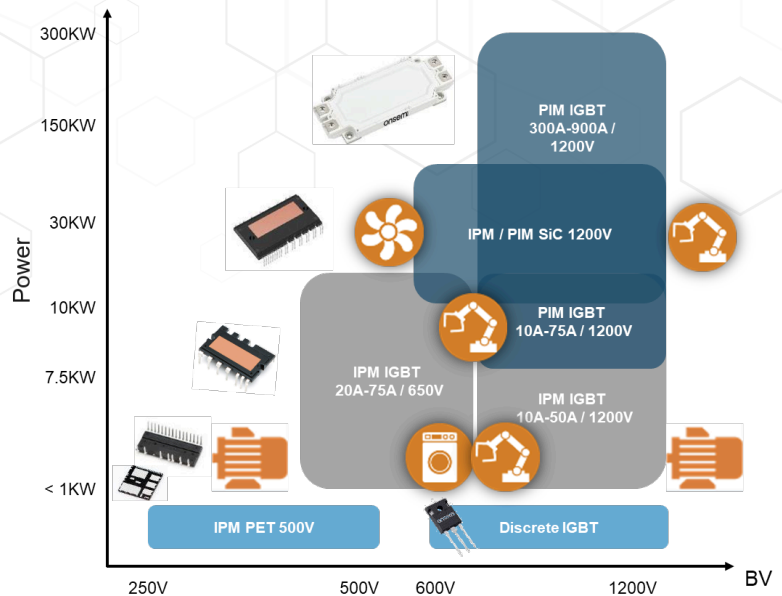


Fig.11: Recommended inverter solution depending on the desired power level and bus voltage

Since modules integrate power components as well as protections (such as UVLO, short-circuit protection, thermal sensing, etc.) they reduce required space and are more reliable since they are fully tested. onsemi offers modules in SiC and IGBT technology in various packages and with numerous topologies and features.

Power integrated modules integrate the discrete output stage and AC/DC converter into a single part. Some of the PIMs integrate a brake, which is why they are known as converter inverter brake (CIB) PIMs. PIMs still require separate and suitable gate drivers.

Intelligent power modules, in addition to the inverter stage, also include gate driver and protection. They greatly reduce the system size and time to market. An example of an onsemi IPM and its elements is illustrated in the figure 12.

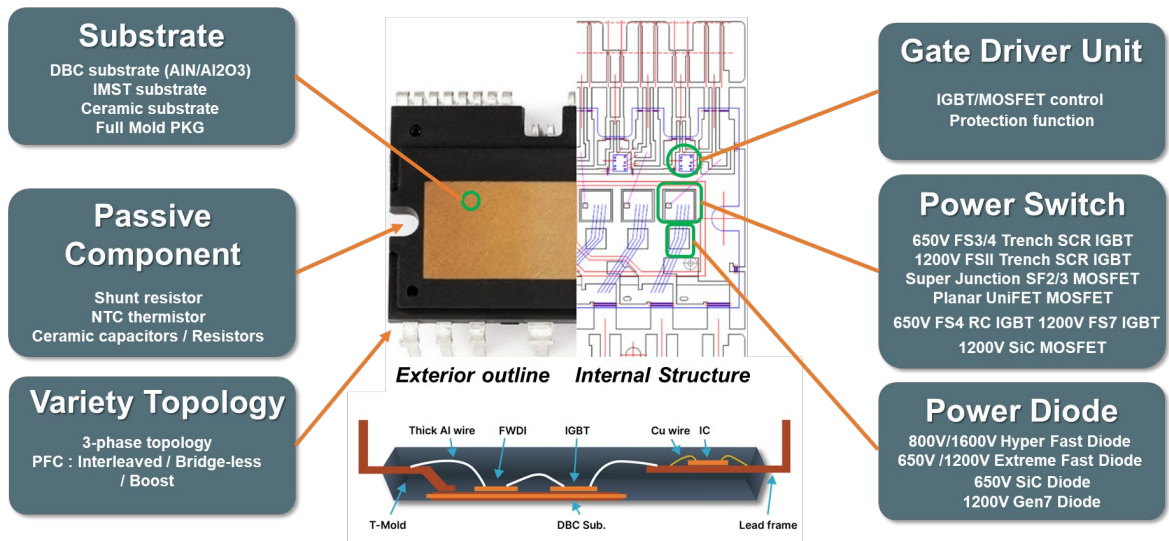


Fig.12: Level of integration of onsemi Intelligent power module

Solution Overview

IGBT – Cost-effective High-voltage Switch

IGBTs are optimal for high-voltage applications, as they provide a higher blocking voltage for equivalent material thickness, compared to the Si MOSFETs. IGBT switches are a cost-effective and mainstream solution. Their disadvantage is that they have a lower possible switching frequency, which means that the used inductors would be larger. IGBTs have a long history of driving motors at frequencies up to 20 kHz.

Field Stop VII, IGBT, 1200V

- New Family of 1200 V Trench Field Stop VII IGBT
- Low $V_{CE(SAT)}$ type for motor control applications – increases the power that can be handled and decreases the power losses generated as heat and thus improves cooling
- Improved parasitic cap for high-frequency operation, high ruggedness
- 1200V Gen7 diode for low V_F and softness – lower voltage drop decreases the conduction losses and softness refers to the reverse recovery of the diode. The softer is the reverse recovery the less noise and fewer electromagnetic interference (EMI) issues

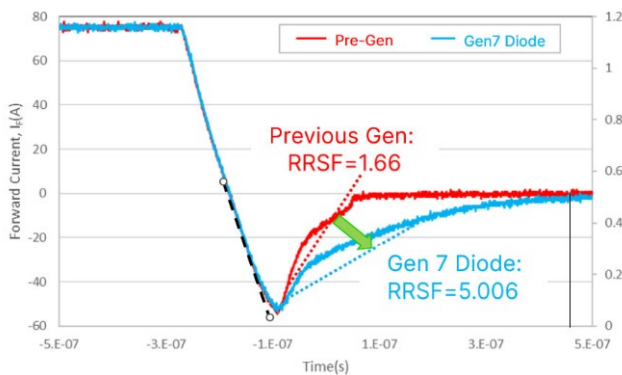


Fig.13: Comparison of softness of Gen7 and previous Gen diode

Diode softness is defined as diode recovery softness factor (RRSF),

$$RRSF = \frac{\left| \frac{dI_{rise}}{dt} \right|}{\left| \frac{dI_{fall}}{dt} \right|}$$

where dI_{rise}/dt is the maximum slope when reverse current rise from 0 to peak during turn-off, dI_{fall}/dt

is the maximum slope the reverse current falls from peak to 0. As Figure 13 shows, latest Gen7 diode has softness of 5, three times improved than previous generation. See more in [Advanced Industrial Motor Control for Increased Power Efficiency](#).

IGBT FGY100T120RWD

- 1200V, 100A IGBT from FS7 family
- Integrated Gen7 diode
- $V_{CE(SAT)} = 1.4V$, $T_{jmax} = 175^{\circ}C$
- Positive temperature coefficient for easy parallel operation
- Low conduction loss and optimized switching for motor control applications

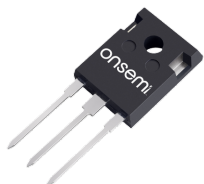


Fig.14: TO-247-3 package

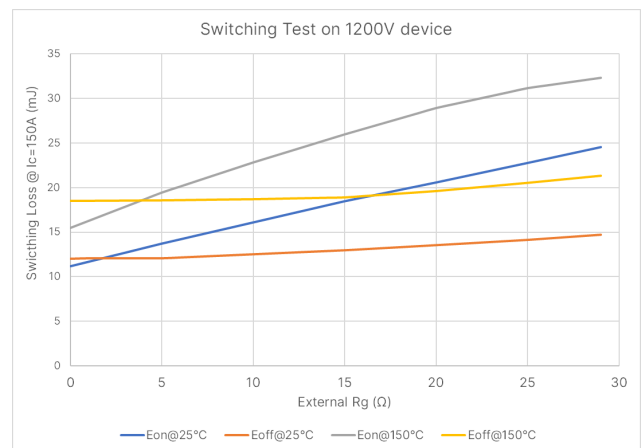


Fig.15: Switching losses of 1200V IGBT from FS7 family

Solution Overview

EliteSiC MOSFET – Best Performance

The SiC MOSFETs offer the best performance for applications requiring high voltage and high frequencies. Silicon carbide is a wide band gap semiconductor. Due to inherent material properties such as higher electron mobility, lower intrinsic carrier concentration, and higher thermal conductivity. The comparison between the material can be seen in Table 3. Compared to silicon, SiC MOSFETs offer higher current densities, reduced switching losses, and simplified cooling systems. The efficiency of the system using SiC technology is improved by reducing conduction losses. EliteSiC is the brand name of onsemi's SiC technology. The EliteSiC MOSFETs are available with a breakdown voltage ranging from 650V to 1700V. All families of EliteSiC SiC MOSFETs exhibit no drift in $R_{DS(ON)}$, V_{TH} , or diode-forward voltage over a lifetime due to a special planar design.

SiC MOSFET [NTH4L014N120M3P](#)

- EliteSiC MOSFET from new 1200V M3P Family, ID = 152 A, in TO-247-4L package
- Low switching losses - Typ. EON 1308 μJ at 74 A, 800 V
- $R_{DS(ON)}$ =14 m Ω @ V_{GS} =18 V
- Ultra low gate charge ($Q_G(TOT)$)=137 nC
- High-speed switching with low cap. ($COSS$ =146 pF)



Fig.16: TO-247-4L package

SiC MOSFET [NTH4L023N065M3](#)

EliteSiC MOSFET from new 650V M3S Family

Key Features:

- Improved switching losses
- Optimized for high temperature operation
- $R_{DS(ON)}$ =22.6 m Ω @ V_{GS} =18 V
- Ultra low gate charge ($Q_G(TOT)$)=87 nC
- High-speed switching with low cap. EliteSiC MOSFET from new 650V M3S Family ($COSS$ =153 pF)
- TO-247-4L package

Learn more about M3 family - [AND90204 - onsemi EliteSiC Gen 2 1200 V SiC MOSFET M3S Series](#)

Table 3: Comparison of Silicon and Silicon Carbide material properties

Electrical Property	Silicon	Silicon Carbide
Bandgap (eV)	1.12	3.26
Critical Electric Field (MV/cm)	0.3	3.0
Saturated Electron Velocity ($\times 10^7$ cm/s)	1	2
Thermal Conductivity (W/cm 2 K)	1.3	3.3



Fig.17: Total switching losses comparison at V_{DC} =400V, V_{GS} =18/-3V, R_G =4.7 Ω

Solution Overview

Intelligent Power Modules – Highly Integrated and Reliable

Intelligent Power Module (IPM) is a power switch with the highest degree of integration currently available. The switch is either an IGBT or a Si MOSFET. It is a popular choice for motor control application due to the fact that it is capable of including the entire inverter and PFC stage in a single package. Further advantages include EMI improvements, space optimization and easier thermal design. Refer to figure 19 to see highlights of the onsemi IPM portfolio.

Intelligent Power Module [NFCS1060L3TT](#)

- Fully integrated PFC and inverter stage in one package
- Includes PFC SJ MOSFET, six drive IGBTs
- 600V, 10A
- Built-in over-current and cross-conduction protection
- Built-in bootstrap diodes and NTC
- Reduced PFC inductor size
- Simplified heatsink design
- Reduced EMI

Intelligent Power Module [NFAM3065L4B](#)

- High-performance output stage for ACIM/BLDC/PMSM
- Integrates high side and low side gate drivers, six IGBTs
- 650V, 30A
- Built-in over-current and low voltage protection, thermal monitoring and
- Built-in temperature sensor
- Reduced EMI and losses

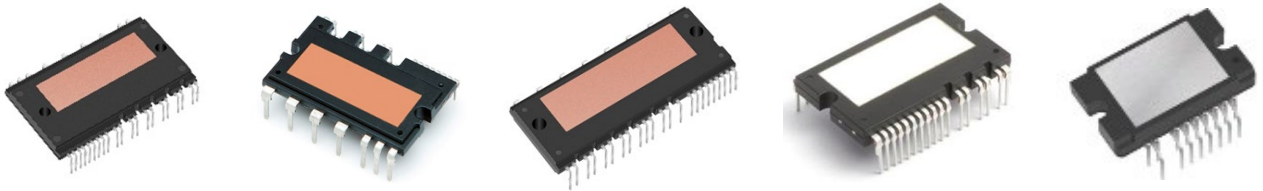


Fig.18: variety of **onsemi** IPM packages

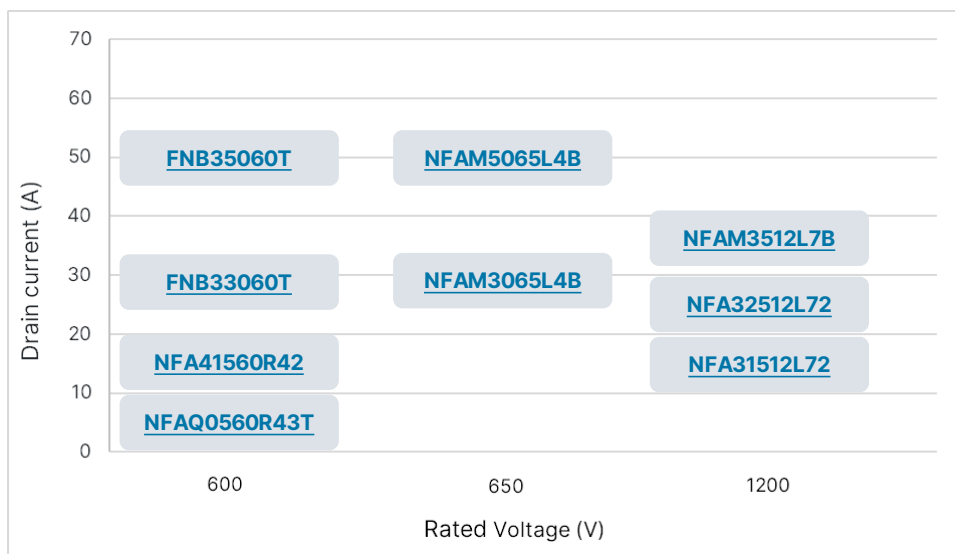


Fig.19: **onsemi** IGBT IPM portfolio

Solution Overview

Power Integrated Modules (PIM) – Highest Power

onsemi offers power integrated modules that utilize SiC MOSFET and IGBT technologies. They enable design improvements and can be used at up to 1200V.

IGBT devices still remain the primary choice due to their high voltage, high current capabilities and lower cost. Their main disadvantage – low switching speed, is of less importance in motor control applications.

SiC devices offer the best performance and power density and are being adopted rapidly. Lower switching losses enable higher efficiency with less cooling efforts or higher switching frequency with reduced size and cost of passive components. These benefits can justify the higher costs of SiC power devices.

PIMs can include half-bridge, full-bridge or even whole three-phase inverter in one package. Using modules greatly reduces design time, cooling size and increases overall integration.

Table 4: Power Integrated Modules for motor control

SiC Half-Bridge (2-Pack) Modules	IGBT Based PIM Modules
Half-Bridge SiC Modules	Available PIM Modules

NXH800H120L7QDSG is a **1200V, 800A rated IGBT Half-Bridge** power module. PIM11 (QD3) Package.

- New Field Stop Trench 7 IGBT technology and Gen. 7 diodes provide lower conduction losses and switching losses, enabling designers to achieve high efficiency and superior reliability.
- NTC thermistor included
- Low inductive layout

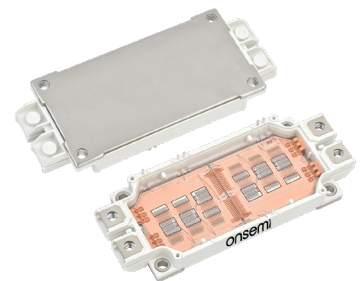
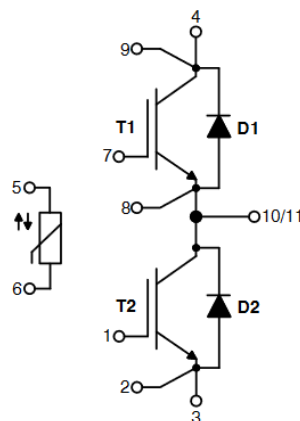


Fig.20: left -NXH800H120L7QDSG schematic, right – PIM11 package

NXH006P120M3F2PTHG is a **1200V SiC Half-Bridge module** in an F2 package.

- M3 EliteSiC technology provides typical $R_{DS(ON)} = 6 \text{ m}\Omega$ at $V_{GS}=18\text{V}$, $I_D = 100\text{A}$.
- Thermistor included
- HPD direct bonded copper substrate

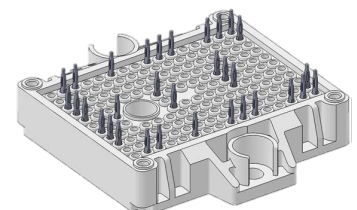
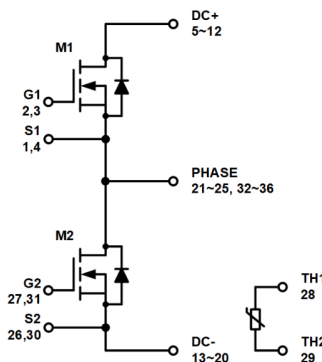


Fig.21: left -NXH006P120M3F2PTHG schematic, right – F2 package

Solution Overview

Elite Power Simulator Powered by PLECS®

PLECS is a system-level simulator that facilitates the modelling and simulation of complete systems with optimized device models for maximum speed and accuracy. PLECS differs from SPICE-based circuit simulators, which focus is on the low-level behavior of circuit components. The PLECS models, referred to as “thermal models”, are composed of lookup tables for conduction and switching losses, along with a thermal chain. During the simulation process, PLECS employs interpolation and extrapolation, using the loss tables to determine the bias point conduction and switching losses associated with the circuit operation.

The [Elite Power Simulator](#) offers a wide range of AC/DC, DC/DC and DC/AC topologies. Additionally, onsemi offers the industry first [Self-Service PLECS Model Generator](#) allowing the user to create custom models which can be used in the Elite Power Simulator.

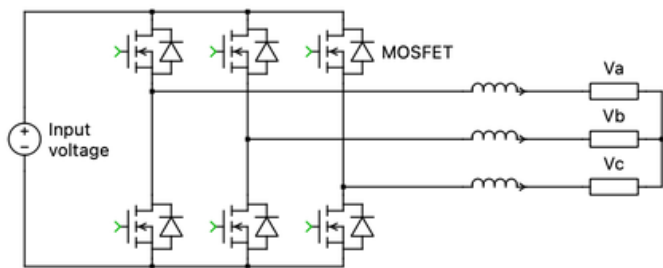


Fig.22: three phase two level inverter topology in Elite Power Simulator

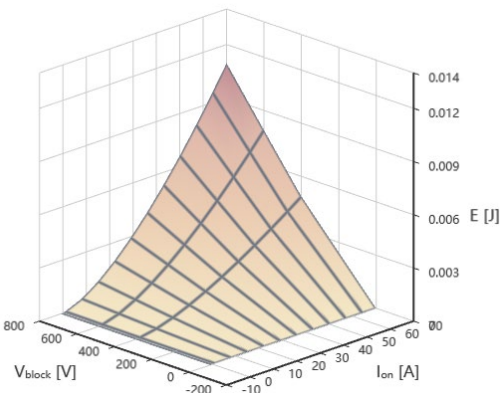


Fig.23: IGBT turn on switch losses @75°C

PLECS offers a range of inverter topologies suitable for industrial motor control including half bridge, full bridge and three-phase inverter.

After selecting the desired topology, the user can modify the voltage and power ratings of the circuit and select a power switch. Currently, PLECS is limited to SiC MOSFETs and power modules, FS7 IGBTs and T10 silicon MOSFETs. Subsequently, the user can observe the losses and thermal data of the device in the graph (figure 23) and in the table.

The simulation results (figures 24 and 25) can be saved and compared to a previous simulation with altered parameters or device. The data from the simulation can be exported and further evaluated.

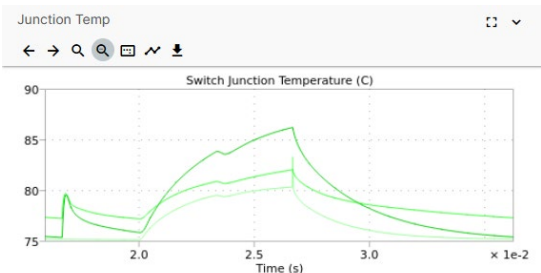


Fig.24: Switch junction temperature comparison @75°C

Losses Breakdown			
	FGHL40T120SWD, Nominal loss data, Trace 1	NXH030P120M3F1PTG, Nominal loss data, Trace 1	NTBG060N090SC1, Nominal loss data
Turn-on Losses	0 W	0 W	0 W
Turn-off Losses	0.32 W	0.01 W	0.01 W
Recovery Losses	0.00 W	0.00 W	0.00 W
Forward Conduction	53.44 W	26.54 W	33.45 W
Reverse Conduction (Body) Diode Conduction (Deadtime)	0 W	0 W	0 W
	1.05 W	2.76 W	3.25 W

Fig.25: Losses breakdown @75°C

Solution Overview

Gate Drivers – Importance of Correct Gate Drive Voltage

The MOSFETs and IGBTs must be driven by the gate drivers as the MCUs, or controllers are unable to drive them directly. The gate driver can be either a single half-bridge, driving one high-side and one low-side switch, or it can incorporate three half-bridge gate drivers, controlling all three motor phases.

It is recommended to use isolated gate drivers for high power applications, as they prevent ground loops that can cause noise. A potential risk to the system's safety arises when the grounding of both circuits is at different potentials. Isolation helps to protect from and safely withstand high voltage surges that could damage equipment or harm humans. It also helps to protect control systems. Furthermore, the isolation helps improving the communication with high-side components in high-voltage solutions.

Table 5: Recommended gate drive voltage

	Si MOSFET/IGBT	SiC MOSFET
Turn-on	10 to 15V	15 to 20V
Turn-off	0V	-2 to -5 V

The operating voltage of the gate drive is determined by the specifications of the power switch. It is imperative that the positive voltage must be high enough to ensure the gate is fully turned on. Additionally, it is crucial to ensure that it does not exceed the maximum gate voltage of the device. When the gate voltage is 0V, it can generally fulfil the turn-off condition for all devices.

The switching losses of SiC MOSFETs can be reduced by utilizing a negative bias during the turn-off phase. This also helps preventing accidental turn-on during turn-off process. Many gate drivers from **onsemi** portfolio support external negative bias, where using external circuit provides negative bias to the gate driver.

The new [NCP51752](#) family has internal negative bias, which saves system costs because the system does not have to supply the negative bias rail to the gate driver. Further information on the benefits of negative gate drive bias can be found in the [onsemi EliteSiC Gen 2 1200 SiC MOSFET M3S Series](#) and in [Choosing the Right Silicon Carbide Gate Driver](#).

Table 6: **onsemi** EliteSiC MOSFETs portfolio and corresponding isolated gate drivers

EliteSiC MOSFETs		1-channel (source/sink)		2-channel (source/sink)	
$V_{(BR)DSS}$	$R_{DS(on)}(typ)$	6.5A/6.5A	4A/6A	6.5A/6.5A	4.5A/9A
650V	12-95mΩ	NCD57090	NCD57000 NCD57001	NCD575xx	NCP51560 NCP51561 NCP51563
750V	13.5mΩ				
900V	16-60mΩ				
1200V	28-960mΩ				

Recommended Products

Suggested Block	Part Number	Description
AC-DC Rectifier		
Si Rectifiers	ISL9R1560P_F085	600V, 15A, 1.65V, TO-220 (2-lead) Stealth™ Rectifier
	ISL9R3060G_F085	600V, 30A, 2.0V, TO-247 (2-lead) Stealth™ Rectifier
	RURG5060_F085	600V, 50A, 1.28V, TO-247 (2-lead) Ultrafast Diode
	Application Recommended Si Rectifiers	
Silicon Carbide (SiC) Diodes	FFSP3065B	SiC Schottky Diode – EliteSiC, 30 A, 650 V, D1, TO-220-2L
	FFSH5065A	SiC Schottky Diode – EliteSiC, 50 A, 650 V, D1, TO-247-2L
	NDSH30120C-F155	SiC Schottky Diode – EliteSiC, 30 A, 1200 V, D3, TO-247-2L
	NDSH50120C	SiC Schottky Diode – EliteSiC, 50 A, 1200 V, D3, TO-247-2L
	Application Recommended SiC Diode	
Power Factor Correction		
Power Factor Controller	FAN9672	Continuous Conduction mode PFC, Interleaved Two-Channel
	FAN9673	Continuous Conduction mode, PFC, Interleaved Three-Channel
	NCP1680	Totem-Pole Critical Conduction Mode (CrM) PFC Controller, up to 350W
	NCP1681	Totem-Pole Continuous Conduction Mode (CCM) / Multi-mode (CrM-CCM) Power Factor Correction Controller, up to 3kW
Intelligent Power Module PFC Combo	NFCS1060L3TT	Intelligent Power Module (IPM), PFC Combo, 600V, 10A
	NFP36060L42T	SPM® 3 27 Series Intelligent Power Module, Bridgeless PFC, 600 V, 60 A
	NFL25065L4BT	PFC SPM® 2 Series for 2-Phase Interleaved PFC
High Voltage MOSFETs	NTHL017N60S5H	N-Channel, SUPERFET® V, FAST, 600 V, 75 A, 17.9 mΩ, TO-247
	NTP125N60S5H	N-Channel, SUPERFET® V, FAST, 600 V, 22 A, 125 mΩ, TO-220
	NTP185N60S5H	N-Channel, SUPERFET® V, FAST, 600 V, 15 A, 185 mΩ, TO-220
	Application Recommended HV MOSFET	
Silicon Carbide (SiC) MOSFETs	NTH4L075N065SC1	SiC MOSFET - EliteSiC, 57 mΩ, 650 V, M2, TO-247-4L
	NTHL023N065M3S	SiC MOSFET - EliteSiC, 23 mΩ, 650 V, M3S, TO-247-3L
	NTBG070N120M3S	SiC MOSFET - EliteSiC, 65 mΩ, 1200 V, M3S, D2PAK-7L
	NTHL040N120M3S	SiC MOSFET - EliteSiC, 40 mΩ, 1200 V, M3S, TO-247-3L
	Application Recommended SiC MOSFET	
IGBT	FGH40T65SQD	IGBT, 650 V, 40 A Field Stop Trench
	FGA60N65SMD	IGBT, 650V, 60A, Field Stop
	FGHL40T120SWD	1200V, 40A Field Stop VII (FS7) Discrete IGBT, TO247-3L
	Application Recommended IGBT	

Recommended Products

Suggested Block	Part Number	Description
Power Factor Correction		
Si Rectifiers	MUR1560	Power Rectifier, Ultra-Fast Recovery, Switch-mode, 15 A, 600 V
	RURG5060-F085	600V, 50A, 1.28V, TO-247 (2-lead) Ultrafast Diode
	Application Recommended Si Diode	
Silicon Carbide (SiC) Diodes	FFSP0665B	SiC Schottky Diode – EliteSiC, 6 A, 650 V, D2, TO-220-2L
	NDSH50120C	EliteSiC, 50 A, 1200 V, D3, TO-247-2L
	Application Recommended SiC Diode	
Inverter Stage		
Intelligent Power Modules	FNB35060T	Intelligent Power Module, 600 V, 50A
	NFAM5065L4B	Intelligent Power Module (IPM), 650V, 50A
	NFAM3512L7B	Intelligent Power Module, SPM31, 1200V, 35A
	NFA32512L72	Intelligent Power Module, 1200V, 25A
	Application Recommended IPM	
Silicon Carbide (SiC) Modules	NXH010P120M3F1PTG	EliteSiC, 10 mΩ SiC M3S, 1200 V, Half Bridge, F1 Package
	NXH010P90MNF1	SiC Module, 2-PACK Half Bridge, 900 V, 10 mΩ SiC M2 MOSFET
	NXH006P120M3F2PTHG	EliteSiC, 6 mΩ SiC M3S, 1200 V, Half Bridge, F2 Package
	Application Recommended SiC Power Module	
Silicon Carbide (SiC) MOSFETs	NTH4L023N065M3S	EliteSiC MOSFET, 23 mΩ, 650 V, M3S, TO-247-4L
	NTH4L014N120M3P	EliteSiC MOSFET, 14mΩ, 1200V, M3P, TO-247-4L
	NTBG014N120M3P	EliteSiC, 14mΩ, 1200 V, M3P, D2PAK-7L
	Application Recommended SiC MOSFET	
IGBT	FGY100T120RWD	1200V, 100A Trench Field Stop VII (FS7) Discrete IGBT
	FGHL40T120RWD	1200V, 40A Trench Field Stop VII (FS7) Discrete IGBT
	FGHL60T120RWD	1200V, 60A Trench Field Stop VII (FS7) Discrete IGBT
	FGH75T65SHDT	IGBT, 650 V, 75 A Field Stop Trench
	Application Recommended IGBT	
IGBT Power Module	NXH800H120L7QDSG	Qdual3 1200 V 800 A Half Bridge IGBT Module
	SNXH800H120L7QDSG	Qdual3 1200 V 800 A Half Bridge IGBT Module for CAV
Stepper Driver		
Motor Drivers, Stepper	NCV70514	Micro-stepping Motor Driver, dual H-bridge, 800mA, SPI
	NCV70517	Micro-stepping Motor Driver, dual H-bridge, 800mA, SPI
	NCV70628	LIN Micro-Stepping Motor Driver 800mA

Recommended Products

Suggested Block	Part Number	Description
Gate Driver		
Three Phase Gate Driver	NCD83591	3-phase, 60V gate driver for motor control applications
	FAN73893	3-Phase Half Bridge Gate Drive IC
	FAN7888	225V, 3.3/5V input logic compatible, 0.65/0.35A sink/source current
	FAN7388	625V, 3.3/5V input logic compatible, 0.65/0.35A sink/source
Half Bridge Si Gate Driver	NCP5104	Single Input High and Low Side Power MOSFET Driver
	NCP5106	MOSFET / IGBT Drivers, High Voltage, High and Low Side
	NCP5111	Power MOSFET / IGBT Driver, Single Input, Half-Bridge
	NCD57252	Isolated Dual-Channel IGBT Gate Driver
	Application Recommended Si/IGBT Half Bridge Gate Driver	
Single Channel Gate Driver	NCP51313	High Side Gate Driver, 130 V, 2.0 A / 3.0 A
	FAN73711	625V,3.3/5V input logic compatible 4/4A sink/source current, High Side
Half Bridge Isolated SiC Gate Driver	NCP51563	5 kVRMS Isolated Dual Channel 4.5/9 A Gate Driver with High Channel-to-Channel Spacing
	NCP51561	5 kVrms Isolated Dual Channel 4.5/9 A Gate Driver
	NCP51560	5 kVrms Isolated Dual Channel 4.5/9 A Gate Driver
	NCD57540	Isolated Dual-Channel Gate Driver with >8mm Creepage and Clearance
Single Isolated SiC Gate Driver	NCD57090	Isolated High Current Gate Driver
	NCD57000	Isolated high current and high gate driver with internal galvanic isolation
	NCD57001	
	NCP51752	3.75 kVRMS, 4.5-A/9-A Isolated Single Channel Gate Driver with Integrated Negative Bias Control
	NCP51152	3.75 kVRMS, 4.5-A/9-A Isolated Single Channel Gate Driver
LLC Converter		
LLC Controller	NCP4390	Resonant Controller with Sync. Rectifier Control, Enhanced Light Load
	NCP13992	Current Mode Resonant Controller with Integrated High Voltage Drivers
	NCP13994	Current Mode Resonant Controller, Active X2
	Application Recommended LLC Controller	
	NCP4305	Sync. Rectification Driver for QR, Forward & LLC
	NCP4306	Sync. Rectification Driver for QR, Forward & LLC
	NCP4307	SR Driver with Dual Vcc and Self-supply for ACF, QR, Forward & LLC
	Application Recommended SR Controller	

Complementary Products

Suggested Block	Part Number	Description
ADC & Isolation		
ADC	NCD98011	12-Bit Low Power SAR ADC Signed Output
	NCD98010	12-Bit Low Power SAR ADC Unsigned Output
Digital Isolation	NCID9411	High Speed Quad-Channel Digital Isolator
	NCID9401	High Speed Quad-Channel Digital Isolator
	NCID9211	High Speed Dual-Channel, Bi-Directional Ceramic Digital Isolator
Auxiliary Power Supply		
Controllers	FAN65008B	Synchronous Buck Regulator, 65V, 10A
	FAN65004B	Synchronous Buck Regulator, 65V, 6A
Offline Controllers	NCP1077	High Voltage Switching Regulator for Offline SMPS
	NCP1253	PWM Controller, Current Mode, for Offline Power Supplies
	NCP1568	AC-DC Active Clamp Flyback PWM Controller
	NCP1239	Fixed Frequency Current Mode Controller for Flyback Converter
	Application Recommended Isolated SMPS	
LDO	NCP189	LDO, 500mA, Low noise, High Accuracy with Power-Good
	NCP164	LDO, 300mA, Ultra-Low Noise, High PSRR with Power-Good
	NCP718	LDO Regulator, 300 mA, Wide Vin, Ultra-Low Iq
	NCP730	LDO Regulator, 150 mA, 38 V, 1 uA IQ, with Power-Good
	Application Recommended LDO	
eFuse	NIS3071	Electronic fuse 4-channel, 8V to 60V, 10A in 5x6mm package
	NIS4461	Electronic fuse (eFuse), 24V, 44mΩ, 4.2A
Interface		
CAN/CAN FD	NCV7344	CAN FD Transceiver, High Speed, Low Power
	NCV7351	CAN/CAN FD Transceiver, High Speed
	NCV7357	CAN FD Transceiver, High Speed
ESD Protection	NUP3125	32V Dual Line CAN Bus Protector in SC-70 (SOT-323)
	NUP3105L	32V Dual Line CAN Bus Protector in SOT-23
	ESD7004	ESD Protection Diode with Low Capacitance
	ESD7504	ESD Protection, USB3.0 ESD Protection Array
	ESD7205	Low Capacitance ESD Protection Diodes for High Speed Data Lines
Ethernet Controllers	NCN26010	Ethernet Controller, 10 Mb/s, Single-Pair, MAC + PHY, 802.3cg, 10BASE-T1S Compliant
	NCN26000	10BASE-T1S Ethernet PHY with MII interface

Complementary Products

Suggested Block	Part Number	Description
Memory		
EEPROM	CAT24C04	EEPROM Serial 4-Kb I2C
	CAT24C128	EEPROM Serial 128-Kb I2C
	CAT24M01	EEPROM Serial 1-Mb I2C
	CAT25080	EEPROM Serial 8-Kb SPI
	CAT25640	EEPROM Serial 64-Kb SPI
	CAT25M01	EEPROM Serial 1-Mb SPI
Flash Memory	LE25U20AMB	Serial Flash Memory, 2 Mb (256k x 8)
	LE25U40CMC	Serial Flash Memory, 4 Mb (512K x 8)
	LE25S161	Serial Flash Memory, 16 Mb (2048K x 8)
SRAM	N01S818HA	Serial SRAM Memory, Ultra-Low-Power, 1 Mb, 1.7 - 2.2 V
	N25S818HA	Serial SRAM Memory, 256-kb, 1.8 V
	N64S830HA	Serial SRAM Memory, 64-kb, 3.0 V
Current & Voltage Sense		
Current Sense Amplifier	NCS21673 NCS21674	Current-Shunt Monitors, 40 V Common Mode, Uni-directional, Single/Dual
	NCS21671	Current-Shunt Monitors, Zero-Drift, 40 V Common Mode, Bi-directional, Shutdown
	NCS7030 NCS7031	Current-Shunt Monitors, 80 V Common Mode, Uni-directional
	NCS7041	Current-Shunt Monitors, 80 V Common Mode, Bi-directional
	NCS210R NCS211R NCS213R NCS214R	Current Sense Amplifier, 26V, Low-/High-Side Voltage Out, Bidirectional Current Shunt Monitor
Voltage Sense	NCS2003	Operational Amplifier, High Slew Rate, Low Voltage, Rail-to-Rail Output
	NCS21801	Operational Amplifier, 10µV, Zero-Drift, 1.8V to 5.5V Supply, 1.5 MHz
	NCS21914	Precision Quad Operational Amplifier, 2 MHz Bandwidth, Low Noise, Zero-Drift, 25 µV Offset
	Application Recommended Voltage Sense Amplifier	
Inductive Sensing		
Inductive Sensor	NCS32100	Industrial Rotary Position Sensor – 6000 RPM full accuracy, 50 arcsec accuracy
	NCV77320	Inductive Position Sensor Interface, linear and angular, SPI
Temperature Sensing		
Temperature Sensor	NCT72	±1°C Temperature Monitor with Series Resistance Cancellation
	N34TS108	Low-voltage Digital Temperature Sensor
	NCT375	Digital Temperature Sensor with 2-wire Interface and SMBus Time-Out

Development Tools and Resources

Product Recommendation Tools+

Utilize our PRT+ tool to identify the ideal onsemi product for your application.

[Find Products](#)

Self-Service PLECS Model Generator

Increase accuracy and improve circuit performance.

[Generate Model](#)

WebDesigner+

Utilize WebDesigner+ to design a power supply tailored to your specific requirements.

[Generate & Optimize](#)

Simulation/SPICE Models

Our SPICE Models will take your simulation results to the next level.

[Search & Download](#)

Interactive Block Diagrams

Create your own bill of materials worksheet today.

[Explore Diagrams](#)

Evaluation/Development Tools

Explore our wide range of evaluation tools.

[Find & Order](#)

Elite Power Simulator

Get valuable insights and accelerate your power device simulation development.

[Simulate Now](#)



Technical Documentation

Name	Description and Link
Whitepaper	DC Motor Driver Fundamentals
Webinar	How to optimize your industrial drives and pumps
Whitepaper	Stepping Motors and Stepping Motor Control System
Whitepaper	Trapezoidal Control of BLDC Motors
Whitepaper	Advanced Industrial Motor Control for Increased Power Efficiency
Whitepaper	Sensorless Direct Torque and Flux Control with Permanent Magnet Synchronous Motors
Application Note	3-phase Inverter Power Module 1200 V SPM 31 Version 2 Series Application Note
Application Note	onsemi M 1 1200 V SiC MOSFETs & Modules: Characteristics and Driving Recommendations
Application Note	3-phase Inverter Power Module 650 V SPM 49 Series Application Note
Application Note	Smart Power Module, Motion SPM 45 V3 Series User's Guide
Application Note	Paralleling of IGBTs
Application Note	MOSFET Basic
Application Note	IGBT Basic II
Application Note	Effect of Gate-Emitter Voltage on Turn on Losses and Short Circuit Capability
Evaluation Kit	4kW 650V Industrial Motor Control Development Kit with Intelligent Power Module (IPM) and Universal Controller Board (UCB)

Technical Documentation

Name	Description and Link
Application Note	Practical Design Guidelines on the Usage of an Isolated Gate Driver
Application Note	A Guideline on the Usage of an Isolated Gate Driver to Efficiently Drive SiC MOSFETs
Whitepaper	SiC MOSFETs: Gate Drive Optimization
Application Note	Active Miller Clamp Technology
Blog	Choosing the Right Silicon Carbide Gate Driver
Evaluation Board	NCD83591 60V, 3-Phase Gate Driver Demo Board
Tutorial	Elite Power Simulator User Guide
Application Note	Technical Advantages of onsemi's New Elite Power Simulator and Self-Service PLECS Model Generator





Intelligent Technology. Better Future.

Follow us @onsemi



[onsemi.com](https://www.onsemi.com)

onsemi, the onsemi logo, and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "onsemi" or its affiliates and/or subsidiaries in the United States and/or other countries. onsemi owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of onsemi's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. onsemi reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and onsemi makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does onsemi assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using onsemi products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by onsemi. "Typical" parameters which may be provided in onsemi data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. onsemi does not convey any license under any of its intellectual property rights nor the rights of others. onsemi products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use onsemi products for any such unintended or unauthorized application, Buyer shall indemnify and hold onsemi and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that onsemi was negligent regarding the design or manufacture of the part. onsemi is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.